
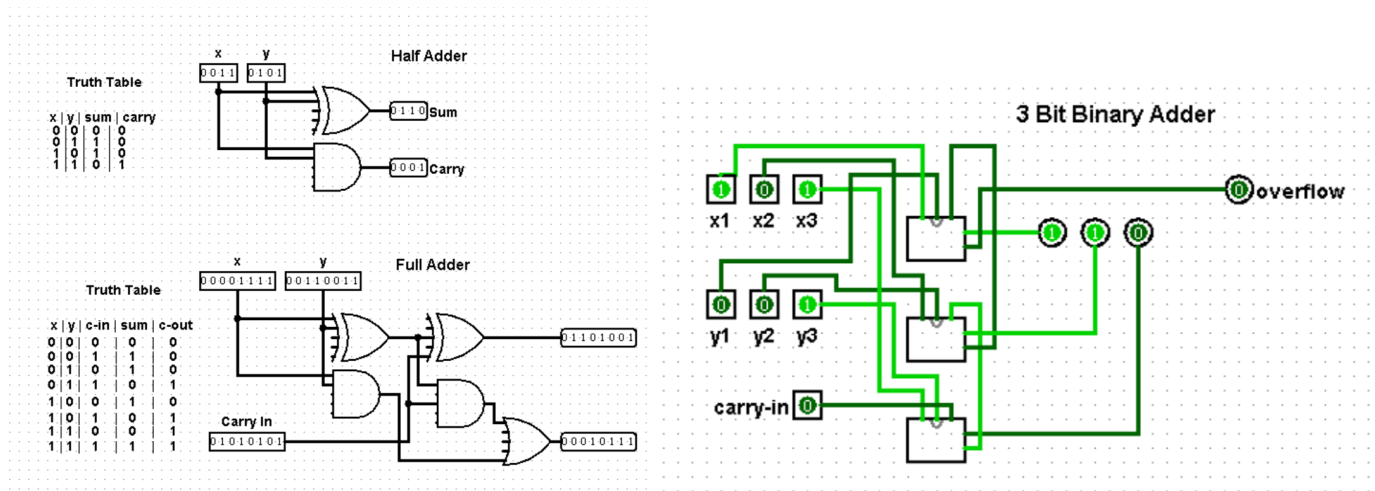


Brandon Perez - Lab 4 Part 1

Main

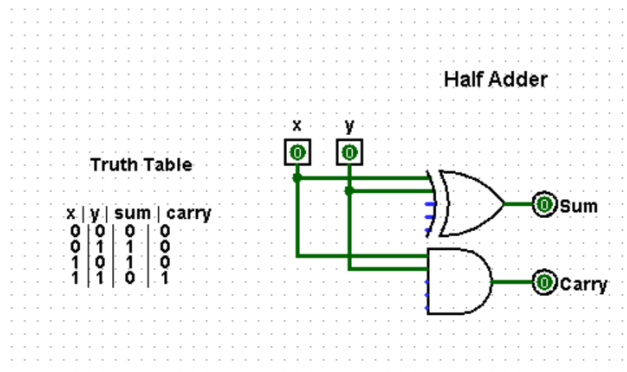

Half Adder Subcircuit



Full Adder Subcircuit

