

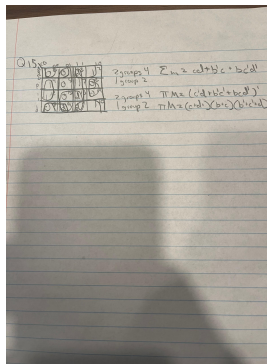
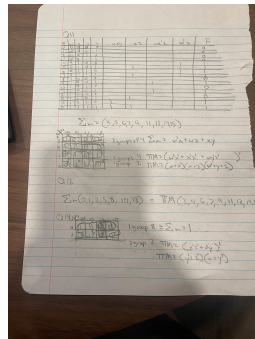
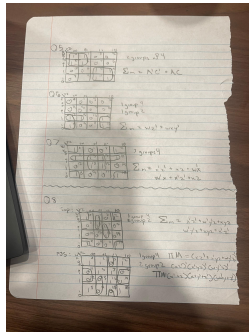


Brandon Perez
Logic Design - Homework 3

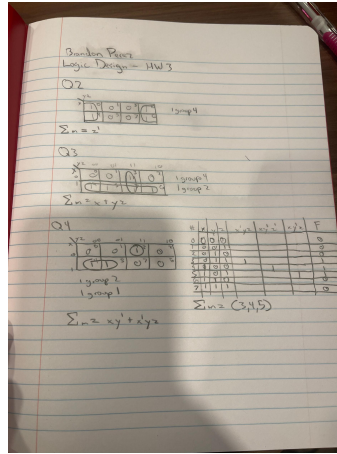

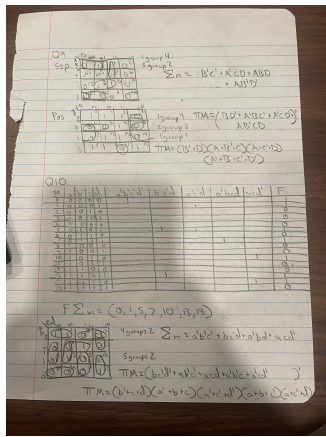Question 13

$$F = (A \text{ xor } B)'(C \text{ xor } D)$$

